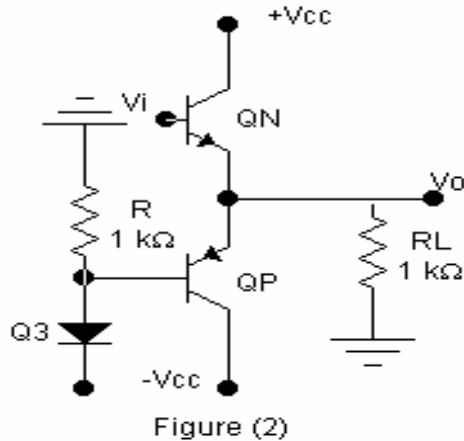
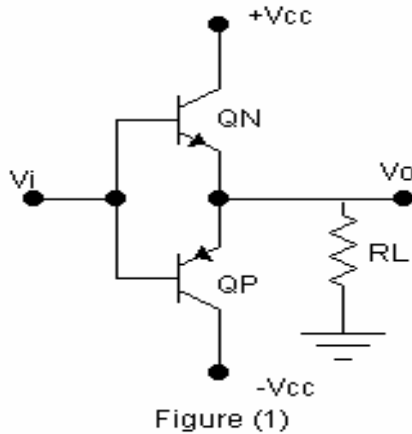




Sheet (2) : Analog ICs ELE221  
 Power Amplifiers

- 1- For the class B output stage of figure (1) let  $V_{cc} = 6V$  and  $R_L = 4 \Omega$ , if the output is sinusoid with 4.5 V peak amplitude, find :
- output power
  - the average power drawn from each supply
  - the power efficiency obtained at this output voltage
  - the peak currents supplied by  $V_i$ , assuming that  $\beta_N = \beta_p = 50$
  - the maximum power that each transistor must be capable of dissipating safely



- 2- A class A emitter follower, biased using the circuit shown in figure (2), all transistors are identical. Assume  $V_{BE} = 0.7V$ ,  $V_{CEsat} = 0.3 v$ , and  $\beta$  very large.
- For linear operation, what are the upper and lower limits of output voltage?
  - and the corresponding inputs?
  - How do these values change if the emitter base junction area of  $Q_3$  is made twice as big as that of  $Q_P$ ? Half as big?
- 3- A source-follower circuit using enhancement NMOS transistors is constructed following the pattern shown in figure (2). All transistor are identical with  $V_t = 1V$  and  $\mu_n C_{ox} W/L = 20 \text{ mA/V}^2$ . For linear operation what are the upper and lower limits of the output voltage, and the corresponding inputs?
- 4- Consider the feedback configuration with class B output shown in figure (3). Let  $A_o = 100 \text{ V/V}$ . Derive an expression for  $V_o$  versus  $V_i$  assuming that  $V_{BE} = 0.7V$ . Sketch the transfer characteristic  $V_o$  versus  $V_i$  and compare it without feedback.

- 5- A class AB output stage, resembling that in figure (4) but with supply of +10 V and biased at  $V_i = 1V$ , is capacitively coupled to a  $100 \Omega$  load.  $V_{BE} = 0.7V$  at 1 mA and for bias voltage of  $V_{BB} = 1.4V$ . What quiescent current results? For a step change in output from 0 to  $-1 V$ , what input step is required ? Assuming transistor saturation voltages of zero, find the largest possible positive and negative-going steps at the output.

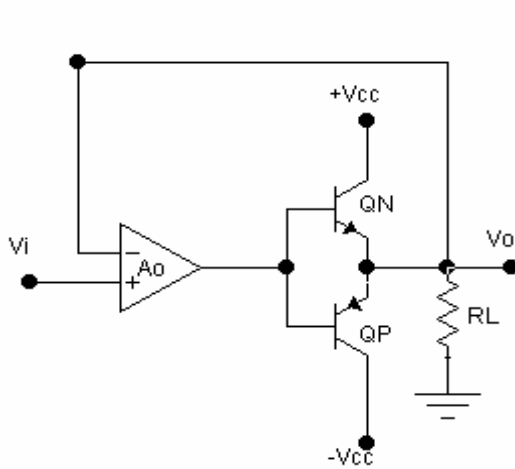


Figure (3)

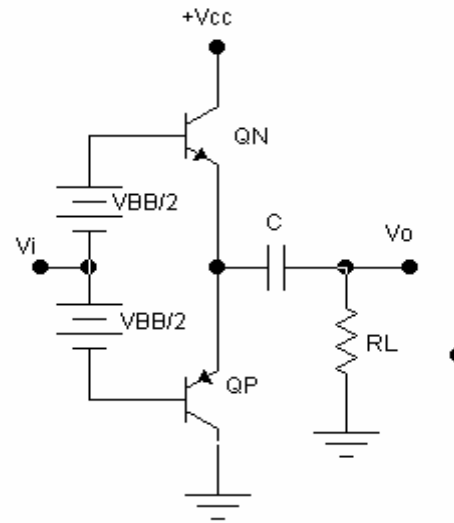


Figure (4)