



Sheet (3) : Analog ICs ELE322
 Oscillators

- 1- In a particular oscillator characterized by the structure of figure (1), the frequency-selective network exhibits a loss of 20 dB and a phase shift of 180° at ω_0 . What is the minimum gain and the phase shift that the amplifier must have for oscillations to begin?

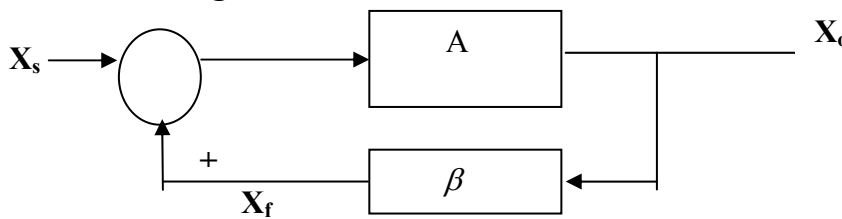


Figure (1)

- 2- For the comparator circuit shown in figure (2) find suitable values for all resistors so that the comparator levels are $\pm 6V$ and so that the slope of the limiting characteristic is 0.1. Use $V_{CC} = 10V$, $V_D = 0.7V$.

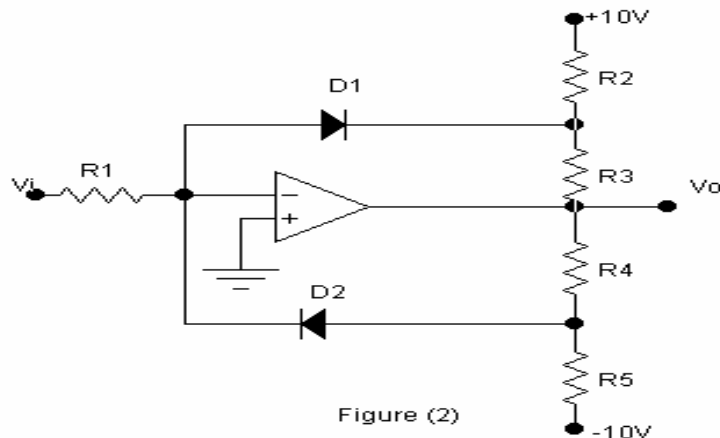


Figure (2)

- 3- For the circuits shown in figure (3) assuming $V_{fwd} = 0.7V$, and Zener voltages to be V_{Z1} and V_{Z2} , sketch and clearly label the transfer function characteristics $V_o - V_i$ assuming ideal op-amps.

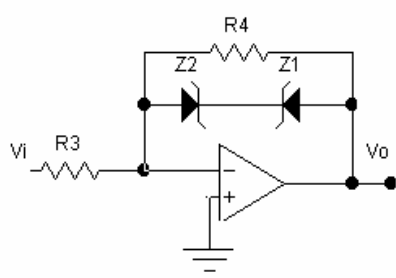


Fig. 3-a

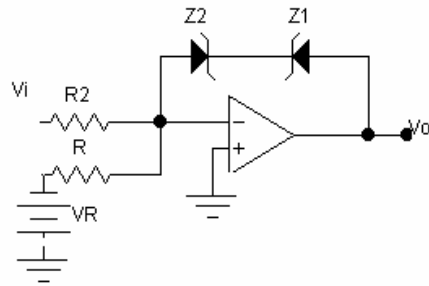


Fig. 3-b

- 4- For the circuit shown in figure (4) find $L(s)$, $L(j\omega)$, the frequency for zero loop phase, and R_2/R_1 for oscillation.

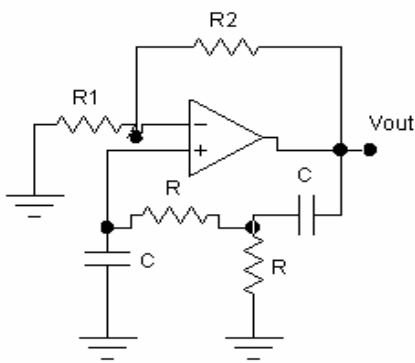


Figure (4)

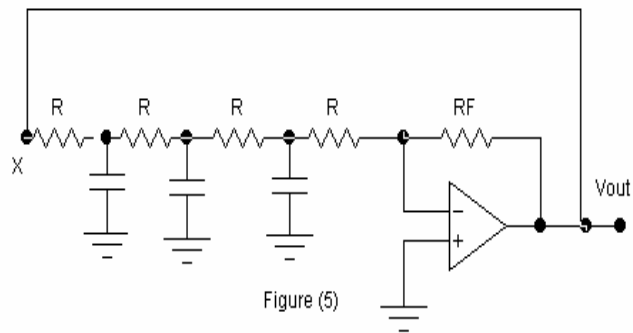


Figure (5)

- 5- For the circuit of figure (5), brake the loop at node X and find the loop gain (working backward for simplicity to find V_x in terms of V_o). For $R = 10 \text{ k}\Omega$, find C and R_f to obtain sinusoidal oscillations at 10 kHz.
- 6- Consider the bistable circuit of figure (6)
- Derive expressions for the threshold voltages V_{TL} and V_{TH} in terms of op-amp saturation levels L_+ and L_- , R_1 , R_2 and V_R .
 - If $L_+ = -L_-$, $R_1 = 10 \text{ k}\Omega$, find R_2 and V_R that results in the threshold voltages of 0 and $V/10$.

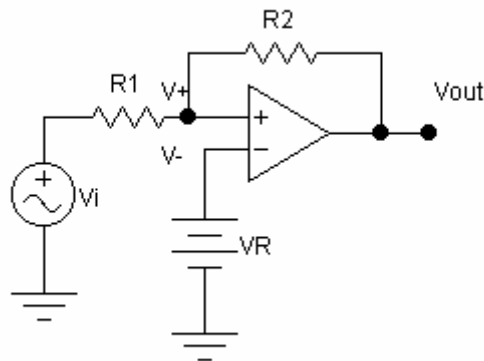


Figure (6)

- 7- Figure (7) shows a monostable multivibrator circuit. In the stable state, $V_o = L+$, $V_A = 0$, and $V_B = -V_{ref}$. The circuit can be triggered by applying a positive input impulse of hight greater than V_{ref} . For normal operation $C1R1 \ll CR$. Show the resulting waveforms of V_o and V_A . Also, show that the pulse generated at the output will have a width T given by

$$T = CR \left(\frac{L_+ - L_-}{V_{ref}} \right)$$

- 8- Consider the 555 circuit of figure (8) when the threshold and the trigger input terminals are joined together and connected to an input voltage V_i . Verify that the transfer characteristic $V_o - V_i$ is that of an inverting bistable circuit with thresholds $V_{TL} = 1/3 V_{CC}$ and $V_{TH} = 2/3 V_{CC}$ and output levels of 0 and V_{CC} .

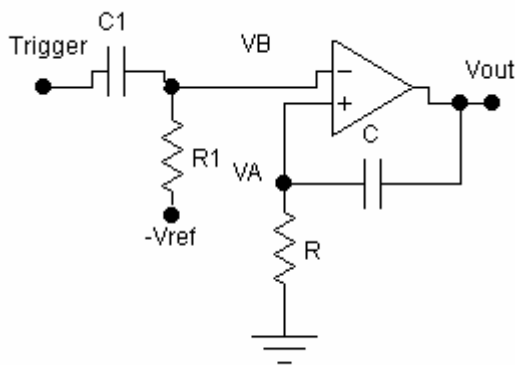


Figure (7)

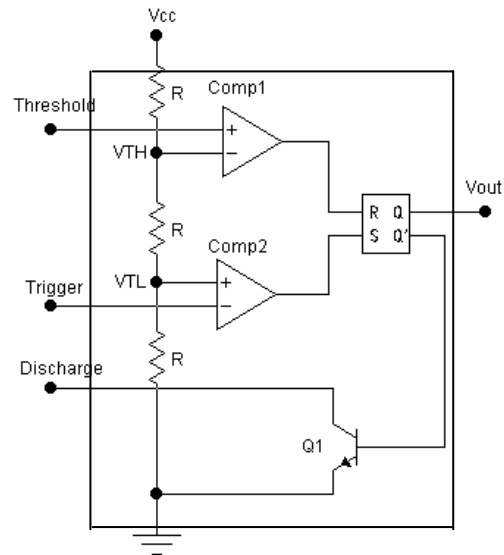


Figure (8)