

# Chapter 3: Sequential Devices


The background features abstract, overlapping geometric shapes in various shades of green, ranging from light lime to dark forest green. These shapes are primarily located on the right side of the slide, with some extending towards the center. The overall aesthetic is clean and modern.

- Sequential circuits, unlike combinational ones whose outputs depend only on the present inputs, the outputs depend on present as well as past inputs. Sequential circuits would require memory while combinational circuits which are memoryless.
- The building blocks ,main devices, used in designing and implementing sequential circuits are Flop-Flops.


- In this chapter we will:

- Understand the design and working principles of Latches and Flip-Flops.
- Understand the importance and significance of sequential circuits in general.


## Latch vs Register (Flip-Flop)

 

Latch  
Level Sensitive

 

Flip-Flop  
Edge Sensitive



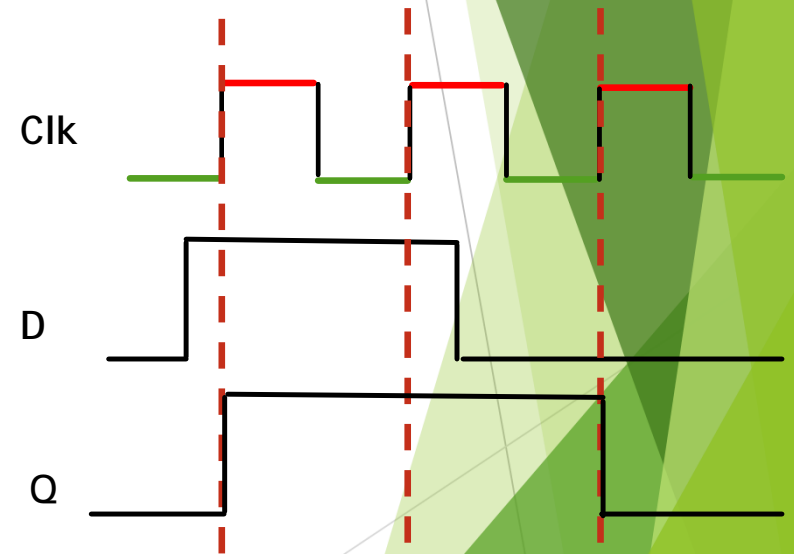


## RS Latch

Inputs		Output	
$R(t)$	$S(t)$	$Q(t)$	$Q(t + \Delta t)$
0	0	0	0
		1	1
0	1	0	1
		1	1
1	0	0	0
		1	0
1	1	0	—
		1	—

$R(t)S(t)$	$Q(t)$			
	00	01	11	10
0	0	1	—	0
1	1	1	—	0

$Q(t + \Delta t)$

   


$$\begin{aligned}
 Q(t + \Delta t) &= S(t) + \overline{R(t)Q(t)} \\
 &= \overline{\overline{S(t)} \cdot R(t)Q(t)}
 \end{aligned}$$

Let us assume the outputs of the forbidden state to be zeros


$R(t)S(t)$		00	01	11	10
		$Q(t)$			
0	0	1	0	0	
1	1	1	0	0	
		$Q(t + \Delta t)$			

$$Q(t + \Delta t) = \overline{R(t)} \cdot [Q(t) + s(t)]$$

$$= R(t) + \overline{[Q(t) + S(t)]}$$

 


 Example: Consider a NAND gate of total delay one unit, get  $z(t + \Delta t)$ .



$$Z(t + \Delta t) = \overline{X(t)Z(t)} = \bar{X}(t) + \bar{Z}(t)$$

Lumped  
delay

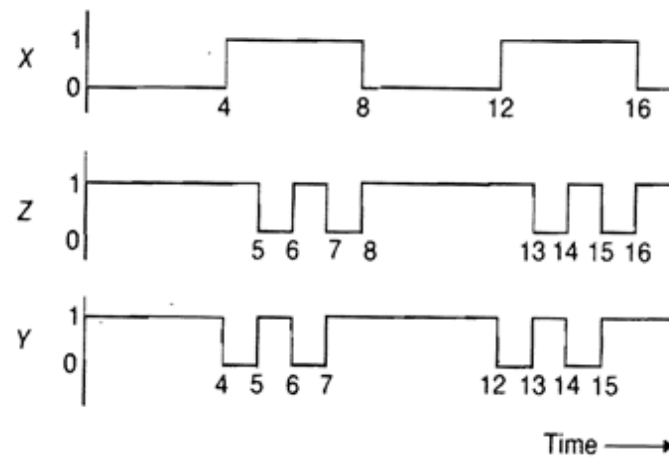

When  $x$  changes from 0 to 1 the output oscillates with a period  $2 \Delta t$ .  
When  $x$  changes from 1 to 0 the output becomes 1 after a delay of  $\Delta t$ .

## Distributed delay

$$Q(t + t_1) = \overline{S(t) \cdot \overline{Q(t)}} = S(t) + Q(t)$$


$$\overline{Q}(t + t_2) = \overline{R(t) \cdot Q(t)} = R(t) + \overline{Q}(t)$$

$$\begin{aligned}\overline{Q}(t + t_1 + t_2) &= \overline{R(t + t_1) \cdot Q(t + t_1)} \\ &= \overline{R(t + t_1) [S(t) + Q(t)]}\end{aligned}$$

$$Q(t + t_1 + t_2) = \overline{R(t + t_1) [S(t) + Q(t)]}$$



$$t_1 = t_2 = \Delta t$$
 
$$Q(t + \Delta t) = \overline{R\left(t + \frac{\Delta t}{2}\right) [S(t) + Q(t)]}$$



gate1 "t<sub>1</sub>" and gate2 "t<sub>2</sub>"

# Timing diagram of the SR latch

 
 





## Clocked SR flip-flop

- Dependable operation of FFs must include clocks
- The Clock input forces an action to take place only when the clock is present, otherwise outputs are forced to remain unchanged

Inputs			Mode	Outputs	
$CK(t)$	$S(t)$	$R(t)$		$Q(t + \Delta t)$	$\bar{Q}(t + \Delta t)$
0	—	—	No action	$Q(t)$	$\bar{Q}(t)$
⌈	0	0	Hold	$Q(t)$	$\bar{Q}(t)$
⌈	0	1	Reset	0	1
⌈	1	0	Set	1	0
⌈	1	1	Invalid	—	—

  

## Maximum Clock Rate

 

$$T_{CK} \geq t_s + t_p + t_{NS}$$

t<sub>s</sub> : setup time, inputs have to be there for some time before triggering

t<sub>h</sub> : hold time, after triggering


t<sub>p</sub> : propagation delay

t<sub>NS</sub> : Delay of Next-State Decoder

$$f_{CK} = \frac{1}{T_{CK}} \leq \frac{1}{t_s + t_p + t_{NS}}$$

Example: Modify the SR flip-flop to accept "11" as a RESET state.



$X(t)$	$Y(t)$	$Q(t)$	$Q(t + \Delta t)$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

KM:

$$Q(t + \Delta t) = X(t)Y(t) + Y(t)Q(t)$$

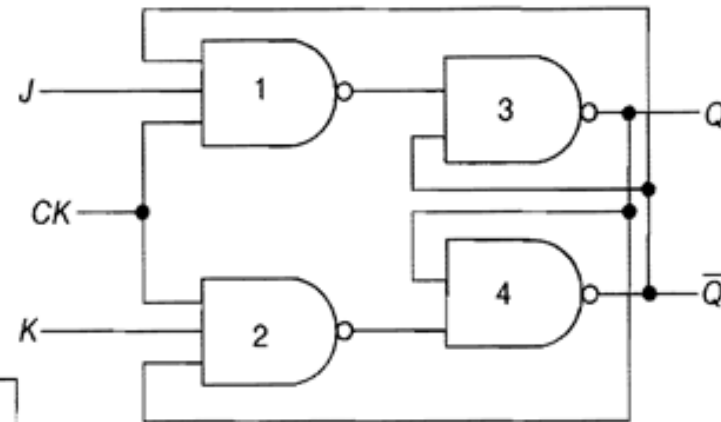
 
An alternative good way is to let the "11" state to make the FF toggle, JK flip-flop




Mode	$J(t)$	$K(t)$	$Q(t)$	$Q(t + \Delta t)$
Hold	0	0	0	0
			1	1
Reset	0	1	0	0
			1	0
Set	1	0	0	1
			1	1
Toggle	1	1	0	1
			1	0

$$Q(t + \Delta t) = J(t)\bar{Q}(t) + \bar{K}(t)Q(t)$$

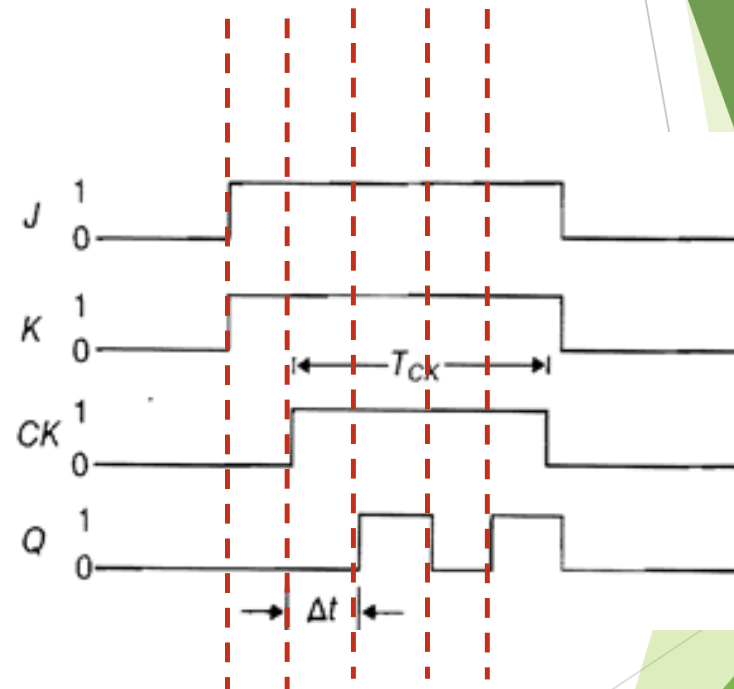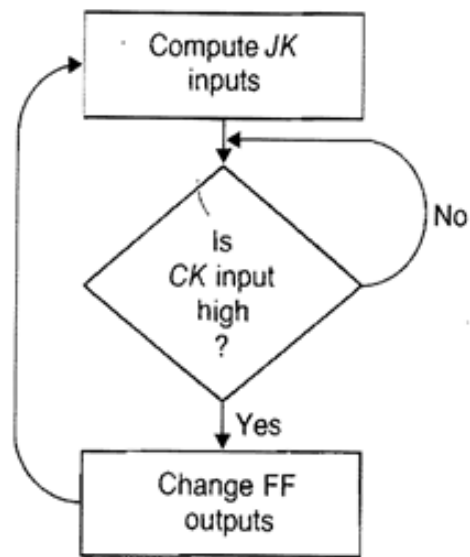The clock period has to be less than the delay of the FF




# Pulse narrowing and edge-triggered FFs

 


Locates the leading edge of the clock

True clock pulse

Inverted delayed clock pulse

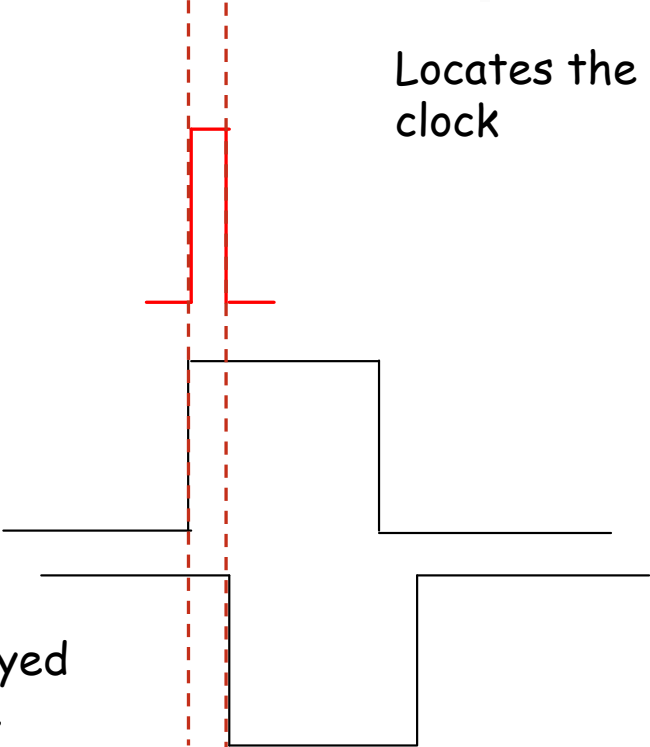



Needed for edge-triggered FFs

 



Example: Obtain the timing diagram for the sequential circuit shown for at least six clock cycles. Assume that  $Q_1(0) Q_2(0) = 00$

$$J_1 = K_1 = Q_2$$

$$J_2 = K_2 = \overline{Q_1}$$

  

  
Obtain the response of the shown circuit, where each of the gates is assumed to have 1 unit of gate delay. The input  $x$  remains high for a duration longer than 5 units.




Locates the trailing edge of the clock



 The memory circuit of sequential circuits is composed mainly of flip-flops.







State diagram

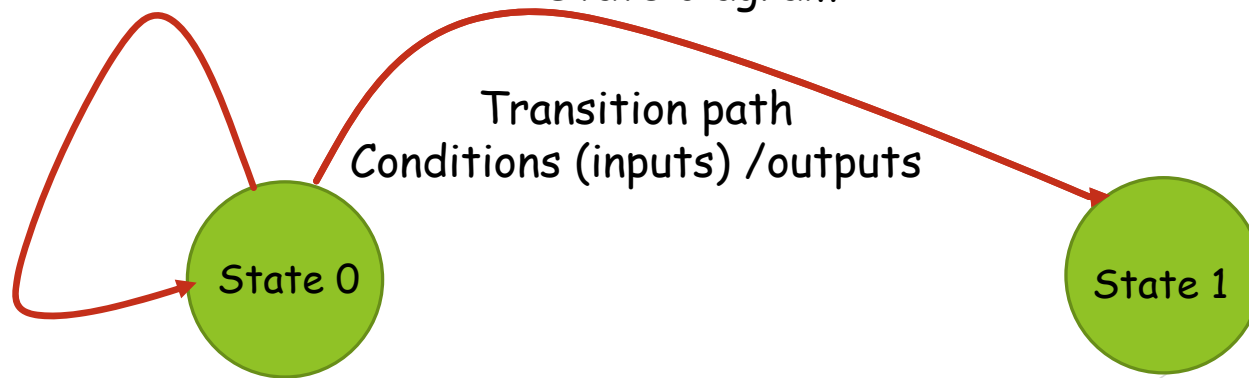


## State diagrams of flip-flops


$Q(t)$	$Q(t + \Delta t)$	$S$	$R$	$J$	$K$	$D$	$T$
0	0	0	—	0	—	0	0
0	1	1	0	1	—	1	1
1	0	0	1	—	1	0	1
1	1	—	0	—	0	1	0

    

## 4-bit parallel (ripple) adder

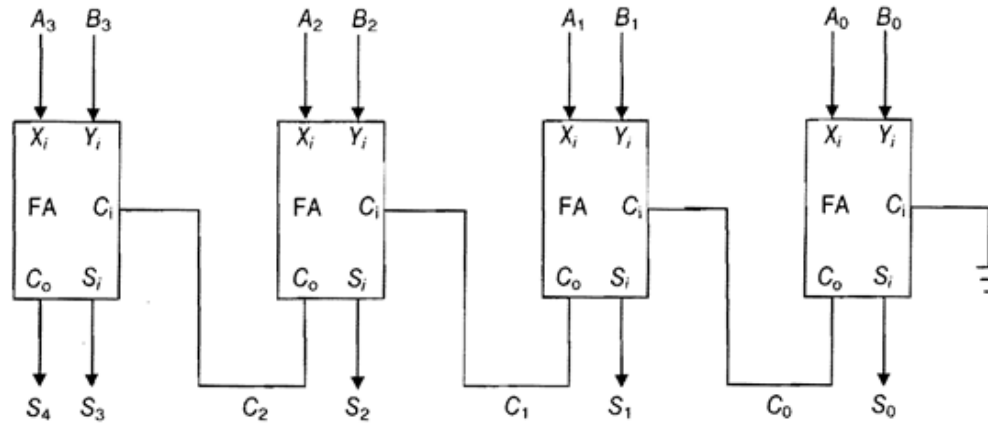

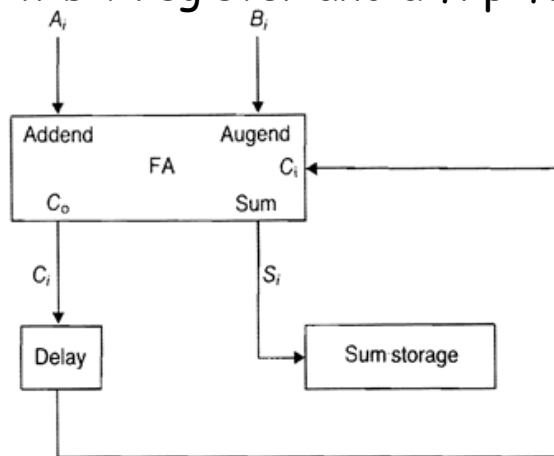n-bit serial adder implemented sequentially by one full adder, n-bit register and a flip-flop




# Chapter 4: Design of Synchronous Sequential Circuits



□ By the end of this chapter we should be able to:


- Differentiate between Mealy and Moore finite-state machines
- Obtain a state diagram for a sequential circuit design
- Follow the different design steps to realize the synchronous sequential machine

## State Diagram and State Table

 


Present state PS	Next state NS, outputs	
	X = 0	X = 1
A	B, 0	A, 0
B	C, 1	A, 0
C	A, 0	B, 0

## Mealy and Moore machines

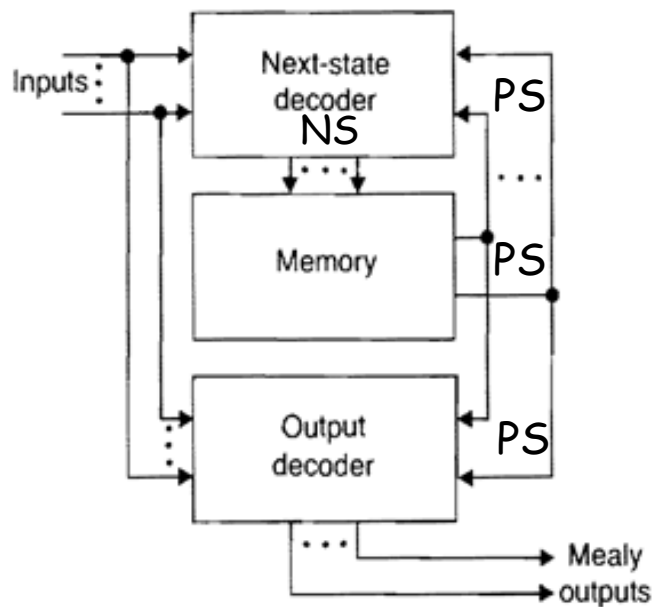


 Outputs depend on both primary inputs and the present state



Outputs depend only on the present state

## State Diagram and State Table

 


PS	NS		Z
	$x = 0$	$x = 1$	
A	C	B	0
B	C	A	1
C	D	C	0
D	A	A	1




Example: Obtain the state diagram of a controller for a serial machine that performs the 2's complement operation .

1100110101010000 ←

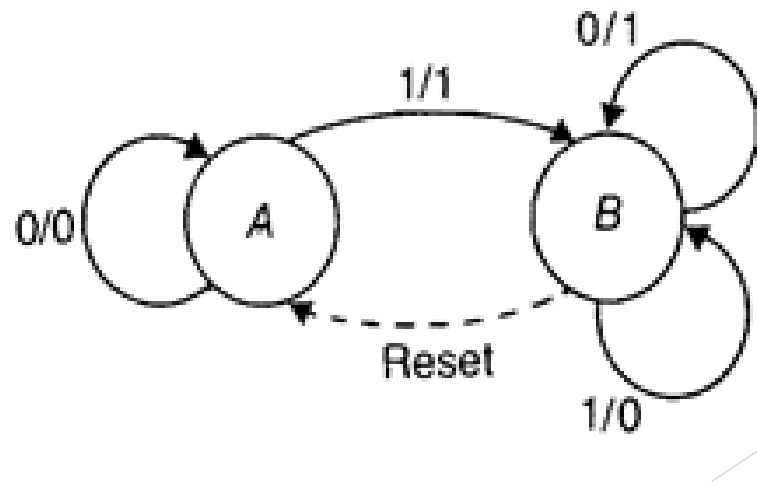

 Example: Obtain the state table for synchronous sequential machine that detects a 01 sequence. The detection of sequence sets the output,  $Z=1$ , which is reset only by a 00 input sequence.



PS	NS, Z	
	x = 0	x = 1
A	B,0	A,0
B	B,0	C,1
C	B,1	C,1


Example: Obtain the Moore equivalent state table for the Mealy machine

PS	NS, Z	
	x = 0	x = 1
A	C,0	A,0
B	B,0	A,0
C	D,1	C,1
D	D,0	B,0
E	C,1	A,0

PS	NS, Z	
	x = 0	x = 1
A	C',0	A,0
B	B,0	A,0
C'	D'',1	C'',1
C''	D'',1	C'',1
D'	D',0	B,0
D''	D',0	B,0
E	C'',1	A,0

PS	NS		Z
	x = 0	x = 1	
A	C'	A	0
B	B	A	0
C'	D''	C''	0
C''	D''	C''	1
D'	D'	B	0
D''	D'	B	1
E	C''	A	—

# Eliminating Redundant States

 

PS	NS		Z
	$x = 0$	$x = 1$	
A	B	C	0
B	A	C	0
C	D	C	0
D	D	E	1
E	A	F	0
F	B	G	0
G	A	E	0

□ Are any two states equivalent? So, do we have any redundant state?

### ❖ Equivalent States:

- Have the same output
- Make the same transition

## Implication Table

<b>B</b>	<b>AB</b>					
<b>C</b>	<b>BD</b>	<b>AD</b>				
<b>D</b>	<b>BD</b> <b>CE</b>	<b>AD</b> <b>CE</b>	<b>CE</b>			
<b>E</b>	<b>AB</b> <b>CF</b>	<b>CF</b>	<b>AD</b> <b>CF</b>	<b>AD</b> <b>EF</b>		
<b>F</b>	<b>CG</b>	<b>AB</b> <b>CG</b>	<b>BD</b> <b>CG</b>	<b>BD</b> <b>EG</b>	<b>AB</b> <b>FG</b>	
<b>G</b>	<b>AB</b> <b>CE</b>	<b>CE</b>	<b>AD</b> <b>CE</b>	<b>AD</b>	<b>EF</b>	<b>AB</b> <b>EG</b>
	<b>A</b>	<b>B</b>	<b>C</b>	<b>D</b>	<b>E</b>	<b>F</b>

PS	NS		Z
	x = 0	x = 1	
<b>A</b>	<b>B</b>	<b>C</b>	<b>0</b>
<b>B</b>	<b>A</b>	<b>C</b>	<b>0</b>
<b>C</b>	<b>D</b>	<b>C</b>	<b>0</b>
<b>D</b>	<b>D</b>	<b>E</b>	<b>1</b>
<b>E</b>	<b>A</b>	<b>F</b>	<b>0</b>
<b>F</b>	<b>B</b>	<b>G</b>	<b>0</b>
<b>G</b>	<b>A</b>	<b>E</b>	<b>0</b>

# Implication Table

B	AB					
C	<del>BD</del>	<del>AD</del>				
D	<del>BD CE</del>	<del>AD CE</del>	<del>CE</del>			
E	<del>AB CF</del>	<del>CF</del>	<del>AD CF</del>	<del>AD EF</del>		
F	<del>CG</del>	<del>AB CG</del>	<del>BD CG</del>	<del>BD EG</del>	AB FG	
G	<del>AB CE</del>	<del>CE</del>	<del>AD CE</del>	<del>AD</del>	EF	AB EG
	A	B	C	D	E	F

PS	NS		Z
	x = 0	x = 1	
A	B	C	0
B	A	C	0
C	D	C	0
D	D	E	1
E	A	F	0
F	B	G	0
G	A	E	0

# Partition Table


F	(FG)
E	(EFG)
D	(EFG)
C	(EFG)
B	(EFG)
A	(AB)(EFG)
<hr/>	
	(AB)(C)(D)(EFG)

B	AB					
C	<del>BD</del>	<del>AD</del>				
D	<del>BD CE</del>	<del>AD CE</del>	<del>DE</del>			
E	<del>AD CE</del>	<del>CF</del>	<del>AD CE</del>	<del>AD EF</del>		
F	<del>CE</del>	<del>AD CG</del>	<del>BD CE</del>	<del>BD EG</del>	AB FG	
G	<del>AD CE</del>	<del>CE</del>	<del>AD CE</del>	<del>AD</del>	EF	AB EG
	A	B	C	D	E	F



## Reduced State Diagram and State Table

(AB)(C)(D)(EFG)

 

n: FFs  
 m: States  
 $m \leq 2^n$

PS	NS		Z
	x = 0	x = 1	
A	B	C	0
B	A	C	0
C	D	C	0
D	D	E	1
E	A	F	0
F	B	G	0
G	A	E	0

PS	NS		Z
	x = 0	x = 1	
A	A	C	0
C	D	C	0
D	D	E	1
E	A	E	0

## State Transition Table

A = 00, C = 01, D = 11, and E = 10

PS $Q_1Q_2$	NS		Z
	$x = 0$	$x = 1$	
00	00	01	0
01	11	01	0
11	11	10	1
10	00	10	0

## Excitation Maps and Design Equations

$Q_1Q_2$	00	01	11	10
X	0	0	1	0
0	0	0	1	0
1	0	0	1	0

Z, output  
 $Z = Q_1Q_2$

$Q_1Q_2$	00	01	11	10
X	0_	1_	_0	_1
0	0_	0_	_0	_0
1	0_	0_	_0	_0

$$J_1K_1$$

$$J_1 = \bar{x}Q_2$$

$$K_1 = \bar{x}Q_2$$


$Q_1Q_2$	00	01	11	10
X	0_	_0	_0	0_
0	0_	_0	_0	0_
1	1_	_0	_1	0_

$$J_2K_2$$

$$J_2 = xQ_1$$

$$K_2 = xQ_1$$

## Hardware Implementation

 

Example: Find the HW implementation of the FSM whose state transition table is given below

PS $Q_1Q_2$	NS	
	$x = 0$	$x = 1$
00	01,0	00,0
01	11,1	00,0
11	00,0	01,0
10	---,-	---,-

$Q_1Q_2$ $x$	00	01	11	10
0	0	1	0	--
1	0	0	0	--

$Z$

$$Z = \bar{Q}_1Q_2\bar{x} \cdot CK$$

$Q_1Q_2$ $x$	00	01	11	10
0	0-	1-	-1	--
1	0-	0-	-1	--

$J_1K_1$

$$J_1 = \bar{x}Q_2$$

$$K_1 = 1$$


$Q_1Q_2$ $x$	00	01	11	10
0	1-	-0	-1	--
1	0-	-1	-0	--

$J_2K_2$

$$J_2 = \bar{x}$$

$$K_2 = \bar{Q}_1x + Q_1\bar{x} = Q_1 \oplus x$$

## Hardware Implementation

 

$$Z = \bar{Q}_1 Q_2 \bar{x} \cdot CK$$

$$J_1 = \bar{x} Q_2$$


$$K_1 = 1$$

$$J_2 = \bar{x}$$


$$K_2 = \bar{Q}_1 x + Q_1 \bar{x} = Q_1 \oplus x$$
 
## Design Algorithm

- Step 1.** Obtain the state diagram from the word statement of the problem.
- Step 2.** Obtain the state table from the state diagram.
- Step 3.** Eliminate the redundant states.
- Step 4.** Make state assignments.
- Step 5.** Determine the type of FFs to use and obtain the corresponding excitation maps.
- Step 6.** Determine the output and FF equations.
- Step 7.** Construct the logic circuit.



 Design a two-bit clocked sequential counter circuit that counts clock pulses.



PS	NS	$Z_1Z_2$
A	B	00
B	C	01
C	D	10
D	A	11

PS	NS	$Z_1Z_2$
$Q_1Q_2$		
00	01	00
01	10	01
10	11	10
11	00	11

$Q_2 \backslash Q_1$	0	1
0	0—	—0
1	1—	—1

$J_1K_1$

$$J_1 = Q_2$$


$$K_1 = Q_2$$

$Q_2 \backslash Q_1$	0	1
0	1—	—1
1	—1	—1

$J_2K_2$

$$J_2 = 1$$

$$K_2 = 1$$

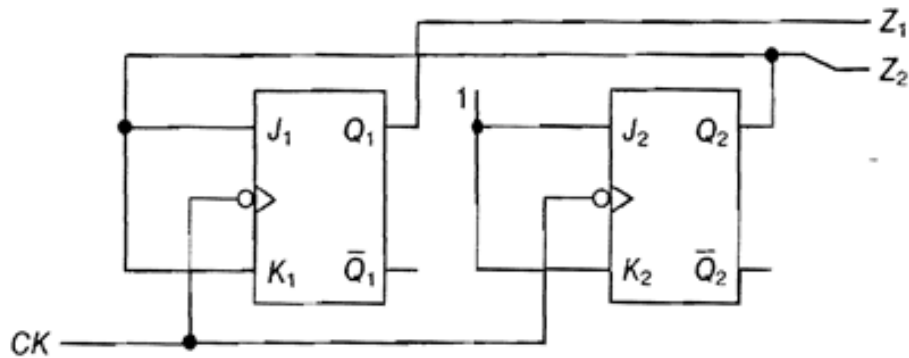



Repeat the design of Example 7.5 by assigning  $A = 00$ ,  $B = 01$ ,  $C = 11$ , and  $D = 10$ . Construct the corresponding timing diagram as well.

PS		
$Q_1Q_2$	NS	$Z_1Z_2$
00	01	00
01	11	01
11	10	10
10	00	11

$Q_1 \backslash Q_2$	0	1
0	0—	—1
1	1—	—0

$J_1K_1$

$$J_1 = Q_2$$

$$K_1 = \bar{Q}_2$$

$Q_1 \backslash Q_2$	0	1
0	1—	0—
1	—0	—1

$J_2K_2$

$$J_2 = \bar{Q}_1$$


$$K_2 = Q_1$$

$Q_1 \backslash Q_2$	0	1
0	00	11
1	01	10


$Z_1Z_2$

$$Z_1 = Q_1$$
 
$$Z_2 = Q_1\bar{Q}_2 + \bar{Q}_1Q_2 = Q_1 \oplus Q_2$$



 Obtain a scale-of-seven up-counter, as shown in the state diagram of Figure 7.31, using *D* FFs and PLA. Assume that the counter is tied to a seven-segment display device.



	$Q_3Q_2$			
$Q_1$	00	01	11	10
0	0	0	0	1
1	0	1	—	1

$D_3$

$$D_3 = \bar{Q}_2Q_3 + Q_1Q_2$$

	$Q_3Q_2$			
$Q_1$	00	01	11	10
0	0	1	0	0
1	1	0	—	1

$D_2$

$$D_2 = Q_1\bar{Q}_2 + \bar{Q}_1Q_2\bar{Q}_3$$

	$Q_3Q_2$			
$Q_1$	00	01	11	10
0	1	1	0	1
1	0	0	—	0

$D_1$



$$D_1 = \bar{Q}_1\bar{Q}_2 + \bar{Q}_1\bar{Q}_3$$

PS	NS
$Q_3Q_2Q_1$	NS
000	001
001	010
010	011
011	100
100	101
101	110
110	000

$$D_1 = \bar{Q}_1\bar{Q}_2 + \bar{Q}_1Q_3$$

$$D_2 = Q_1\bar{Q}_2 + \bar{Q}_1Q_2\bar{Q}_3$$


$$D_3 = \bar{Q}_2Q_3 + Q_1Q_2$$

  

The background features abstract, overlapping green geometric shapes, primarily triangles and polygons, in various shades of green, ranging from light to dark. These shapes are positioned on the right side of the slide, creating a modern, layered effect.

# Chapter 5: Introduction to Counters and Registers

❖ Digital Systems usually have two main units:

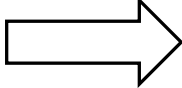➤ A unit for data manipulation  REGISTERS and logic circuits

➤ A second unit for regulating events of the first unit  COUNTERS

❑ Counters:

➤ Synchronous

➤ Asynchronous

❑ Registers:

➤ Serial

➤ Parallel

## Synchronous Binary Counters



Single-bit counter (0, 1, 0, 1,....)  $J = K = 1$

Two-bit counter (00, 01, 10, 11, 00,.....)  $J_1 = K_1 = 1$   
 $J_2 = K_2 = Q_1$

Likewise for three-bit counter  $J_1 = K_1 = 1$   
 $J_2 = K_2 = Q_1$   
 $J_3 = K_3 = Q_2Q_1$

For n-bit counter  $J_n = Q_{n-1}Q_{n-2} \cdots Q_3Q_2Q_1 = Q_{n-1}J_{n-1}$   
 $K_n = Q_{n-1}Q_{n-2} \cdots Q_3Q_2Q_1 = Q_{n-1}K_{n-1}$


# Design a three-bit counter

  


PS	
$Q_3 Q_2 Q_1$	NS
000	001
001	010
010	011
011	100
100	101
101	110
110	111
111	000
 
$$\begin{aligned}
 J_1 &= K_1 = 1 \\
 J_2 &= K_2 = Q_1 \\
 J_3 &= K_3 = Q_2 Q_1
 \end{aligned}$$






Delay and fan-in problems

 


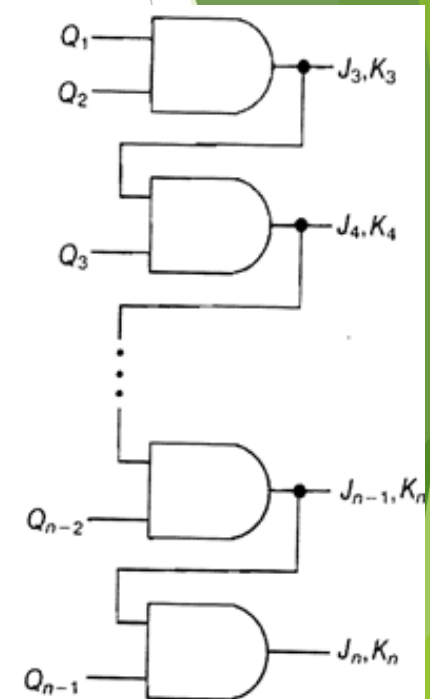- Delay is the same for all stages
- Fan-in problem



 
- Delay increases with stages
- Fan-in is always two.





$E = 1$  for up counting, and  $E = 0$  for down counting

 Obtain the  $J$  and  $K$  equations for a BCD up-counter.



PS	NS	$J_4K_4$	$J_3K_3$	$J_2K_2$	$J_1K_1$
$Q_4Q_3Q_2Q_1$					
0000	0001	0—	0—	0—	1—
0001	0010	0—	0—	1—	—1
0010	0011	0—	0—	—0	1—
0011	0100	0—	1—	—1	—1
0100	0101	0—	—0	0—	1—
0101	0110	0—	—0	1—	—1
0110	0111	0—	—0	—0	1—
0111	1000	1—	—1	—1	—1
1000	1001	—0	0—	0—	1—
1001	0000	—1	0—	0—	—1

	Q <sub>2</sub>			
	0	0	0	0
	0	0	1	0
Q <sub>4</sub> {	-	-	-	-
	-	-	-	-

**J<sub>4</sub>**

	Q <sub>2</sub>			
	0	0	1	0
	-	-	-	-
	-	-	-	-
	0	0	-	-

**J<sub>3</sub>**

	Q <sub>2</sub>			
	0	1	-	-
	0	1	-	-
	-	-	-	-
	0	0	-	-

**J<sub>2</sub>**

	Q <sub>2</sub>			
	1	1	-	1
	-	-	-	-
	-	-	-	-
	1	1	-	-

**J<sub>1</sub>**

	-	-	-	-
	-	-	-	-
	-	-	-	-
Q <sub>4</sub> {	0	1	-	-

Q<sub>1</sub>  
**K<sub>4</sub>**

	-	-	-	-
	0	0	1	0
	-	-	-	-
	-	-	-	-

Q<sub>1</sub>  
**K<sub>3</sub>**

	-	-	1	0
	-	-	1	0
	-	-	-	-
	-	-	-	-

Q<sub>1</sub>  
**K<sub>2</sub>**

	-	-	-	-
	1	1	-	1
	1	1	-	-
	-	-	-	-

Q<sub>1</sub>  
**K<sub>1</sub>**

$$J_4 = Q_1 Q_2 Q_3$$


$$K_4 = Q_1$$

$$J_3 = K_3 = Q_1 Q_2$$

$$J_2 = Q_1 \bar{Q}_4$$

$$K_2 = Q_1$$

$$J_1 = K_1 = 1$$

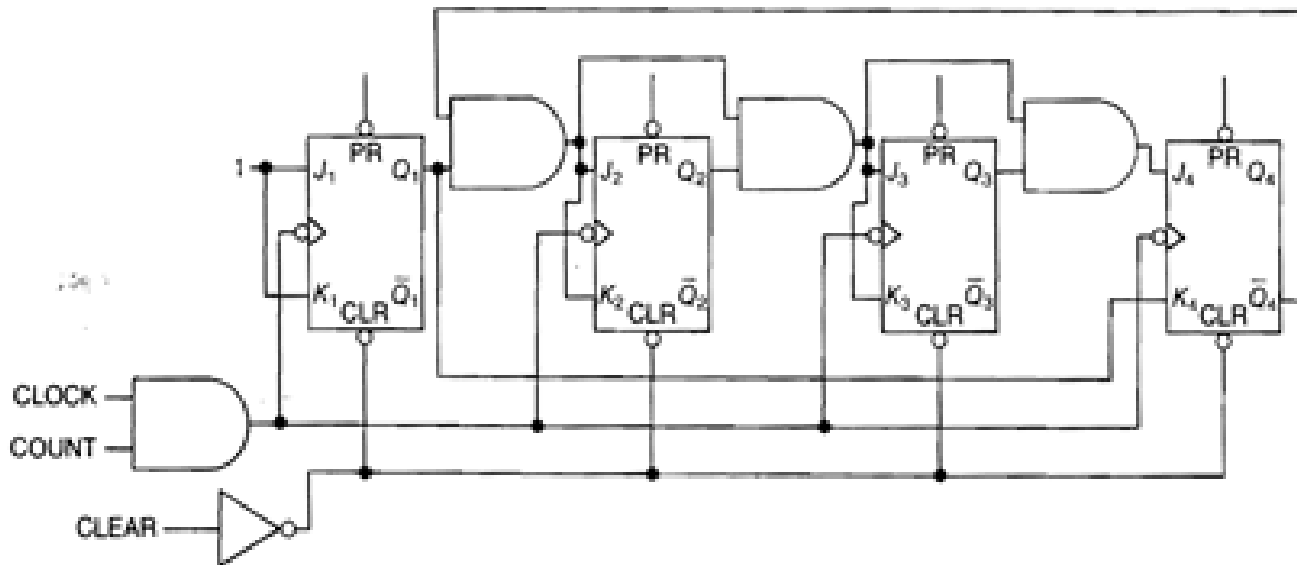

BCD Counter


From a regular 4-bit counter the BCD one can be thought of as such:

1001 should switch to  
0000 and not to  
1010

$Q_4$ , the MSB, should become a 0,  
 $Q_2$  should be prevented from becoming a 1.

$Q_1$  should be fed to  $K_4$ ,  
 $K_4$  and  $J_4$  should not be connected,  
 $Q_1\bar{Q}_4$  should be fed to  $J_2$  and  $K_2$ .

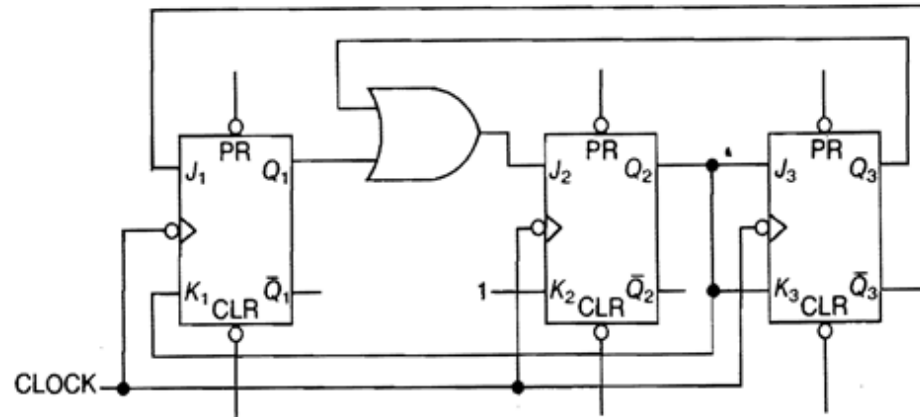Obtain the state table for the counter shown in Figure 10.10, starting from the count 000. The MSB of the count is at  $Q_3$ .



$$\begin{aligned}
 J_1 &= \overline{Q_3}, & K_1 &= Q_2 \\
 J_2 &= Q_1 + Q_3 & K_2 &= 1 \\
 J_3 &= K_3 = Q_2
 \end{aligned}$$

0, 1, 3, 4, 6, 0, .....

PS	$J_3K_3$	$J_2K_2$	$J_1K_1$	NS
000	00	01	10	001
001	00	11	10	011
011	11	11	11	100
100	00	11	00	110
110	11	11	01	000

1  
3  
4  
6  
0

Obtain a synchronous counter that produces the count sequence 0, 2, 4, 3, 6, 7, 0, . . . .

$$J_1 = Q_3$$

$$K_1 = 1$$

$$J_2 = 1$$

$$K_2 = \overline{Q_1 \oplus Q_3}$$

$$J_3 = Q_2$$

$$K_3 = Q_1 + \overline{Q_2}$$

PS	NS			
$Q_3Q_2Q_1$	$Q_3Q_2Q_1$	$J_3K_3$	$J_2K_2$	$J_1K_1$
000	010	0—	1—	0—
001	---	---	---	---
010	100	1—	—1	0—
011	110	1—	—0	—1
100	011	—1	1—	1—
101	---	---	---	---
110	111	—0	—0	1—
111	000	—1	—1	—1

$Q_2Q_1$				
$Q_3$	00	01	11	10
0	0	-	-	0
1	1	-	-	1

$Q_2Q_1$	$J_1$			
$Q_3$	00	01	11	10
0	-	-	1	-
1	-	-	1	-

$K_1$

					00	01	11	10
0	1	-	-	-				
1	1	-	-	-				

					$J_2$			
					00	01	11	10
0	-	-	0	1				
1	-	-	1	0				

$K_2$

					00	01	11	10
0	0	-	1	1				
1	-	-	-	-				

					$J_3$			
					00	01	11	10
0	-	-	-	-				
1	1	-	1	0				

$K_3$



## Hardware Implementation

$$J_1 = Q_3$$


$$K_1 = 1$$

$$J_2 = 1$$


$$K_2 = \overline{Q_1 \oplus Q_3}$$

$$J_3 = Q_2$$

$$K_3 = Q_1 + \overline{Q_2}$$

 


## Asynchronous Binary Counters

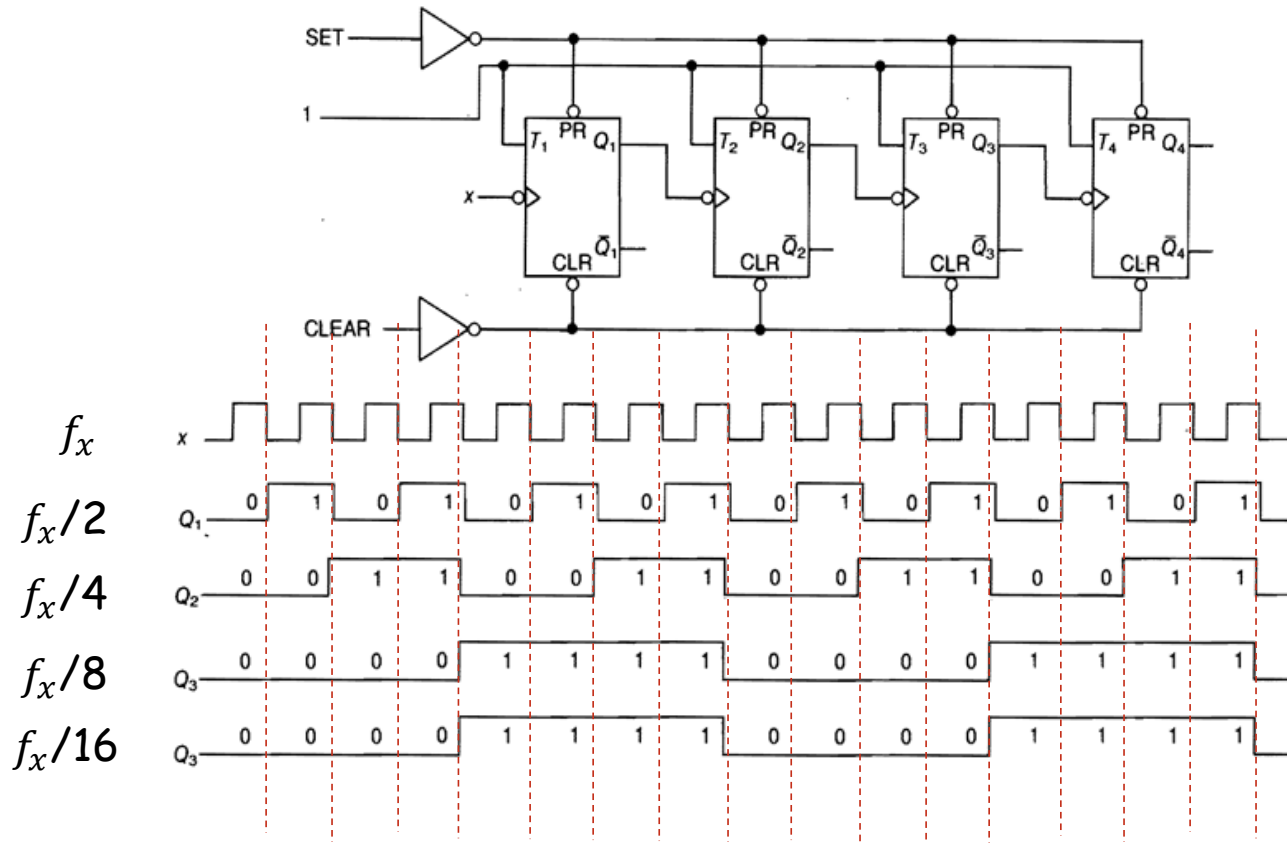

 **Problem :** Timing  
Consequences of a Four-Bit  
Asynchronous Counter During  
1111 → 0000 Transition.

The counter does not go through the transition  
1111 → 0000.

Instead: 1111 → 1110 → 1100 → 1000 → 0000





Total delay for n-bit counter  
is  $nt_f$



Problems:

- Forced regular binary count
- Speed

## BCD Asynchronous Counter

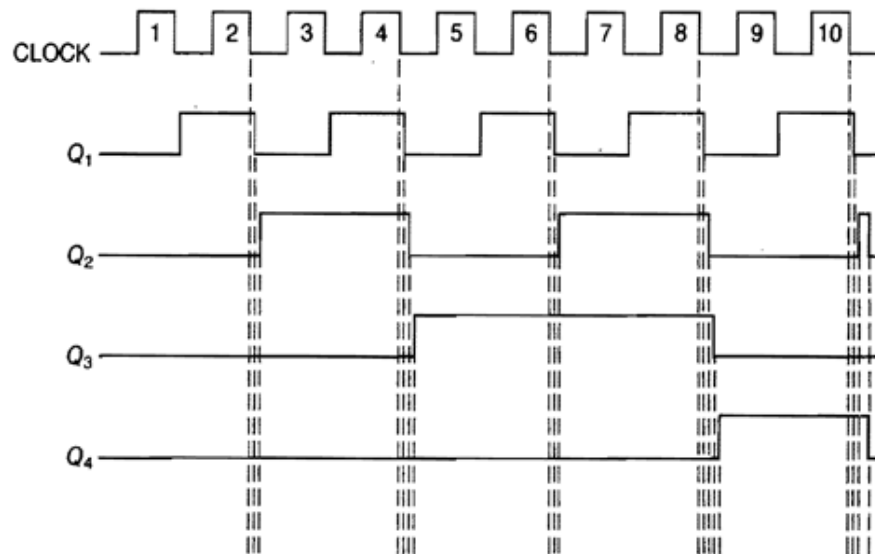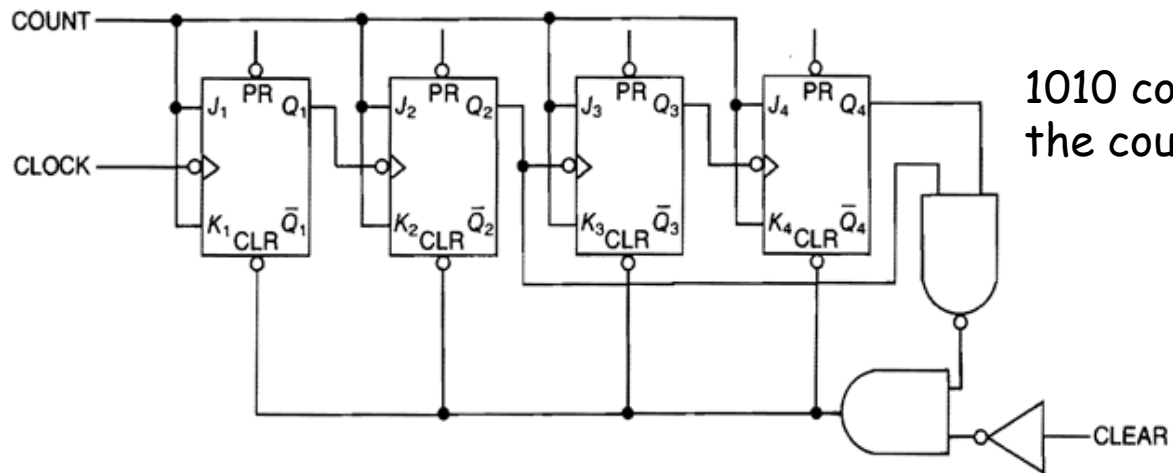

## Integrated Circuit Counter

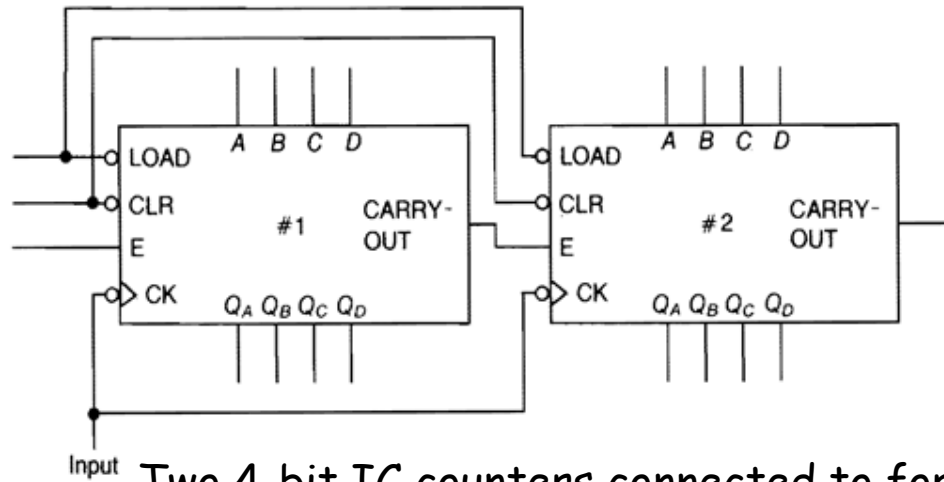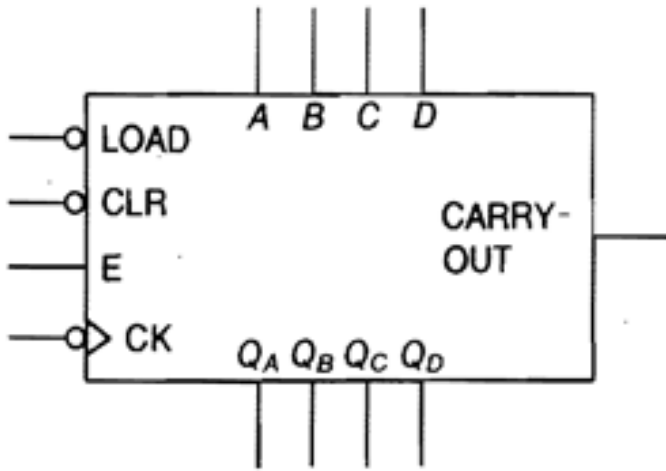

Two 4-bit IC counters connected to form an 8-bit counter

$Q_{D2} Q_{C2} Q_{B2} Q_{A2} \quad Q_{D1} Q_{C1} Q_{B1} Q_{A1}$

0 0 0 0 0 0 0 0

0 0 0 0 0 0 0 1

0 0 0 0 0 0 1 0





⋮

0 0 0 0 1 1 1 1

0 0 0 1 0 0 0 0

Carry out = 1  
E = 1

  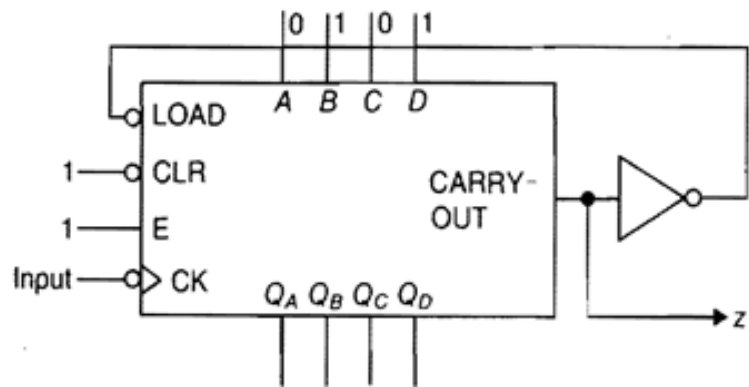 Design a counter using the module of Figure 10.18 that outputs a 1 each time six counts have been received.




The END



## The Basic Shift Register


- LSBs are lost and MSBs are replaced with ones  
Shift-right register
- LSBs replace MSBs  
Circulate-right register
- MSBs replace LSBs  
Circulate-left register
- Shift left one bit = multiply by 2
- Shift right one bit = divide by 2

After Clock	Bit Pattern
0	00101100101
1	10010110010
2	11001011001
3	11100101100
4	11110010110
5	11111001011
⋮	⋮
10	11111111110
11	11111111111

 


 
## Shift-right register Serial-in Serial-out



D FFs


At each clock edge  
Ds are right-shifted  
to Qs

JK FFs

At each clock edge  
JKs are right-shifting  
0 or 1 to Qs

Let it go then HOLD
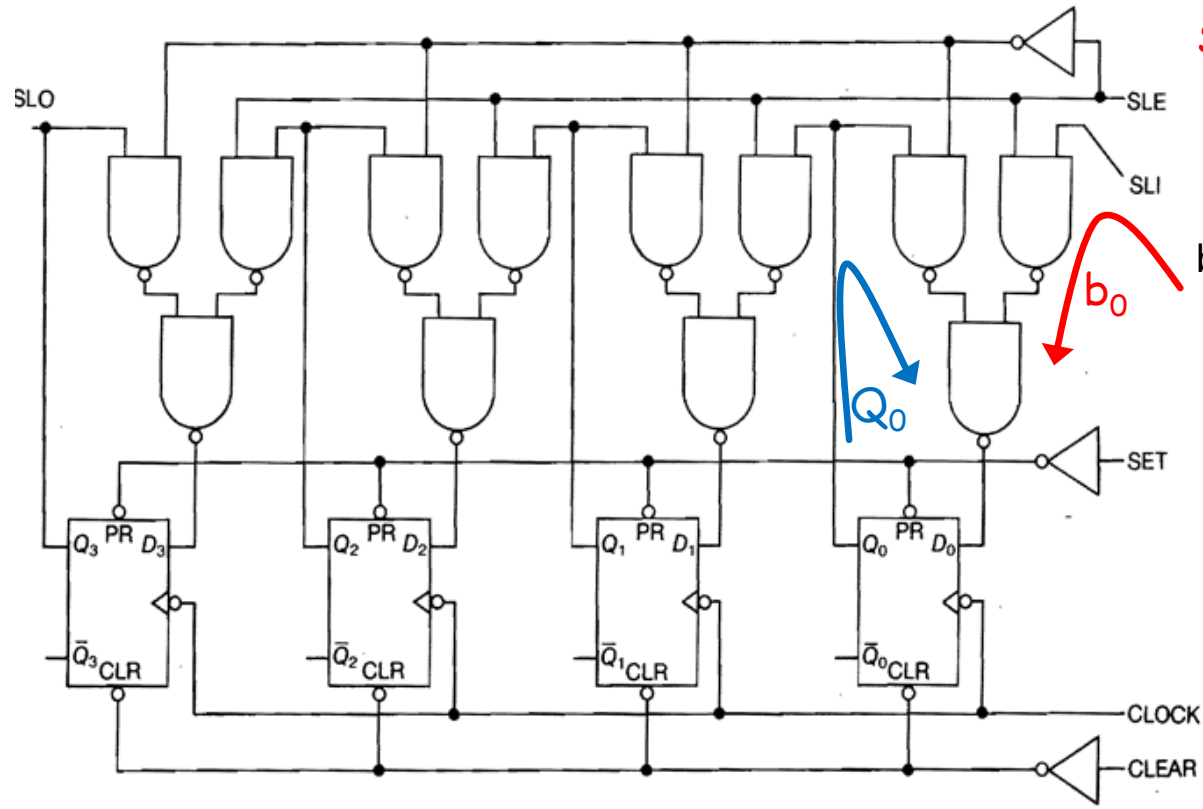
# Shift-left serial-in serial-out register




SLE = 1, shift left

SLE = 0, stores shifted bits

$b_0 b_1 b_2 \dots$

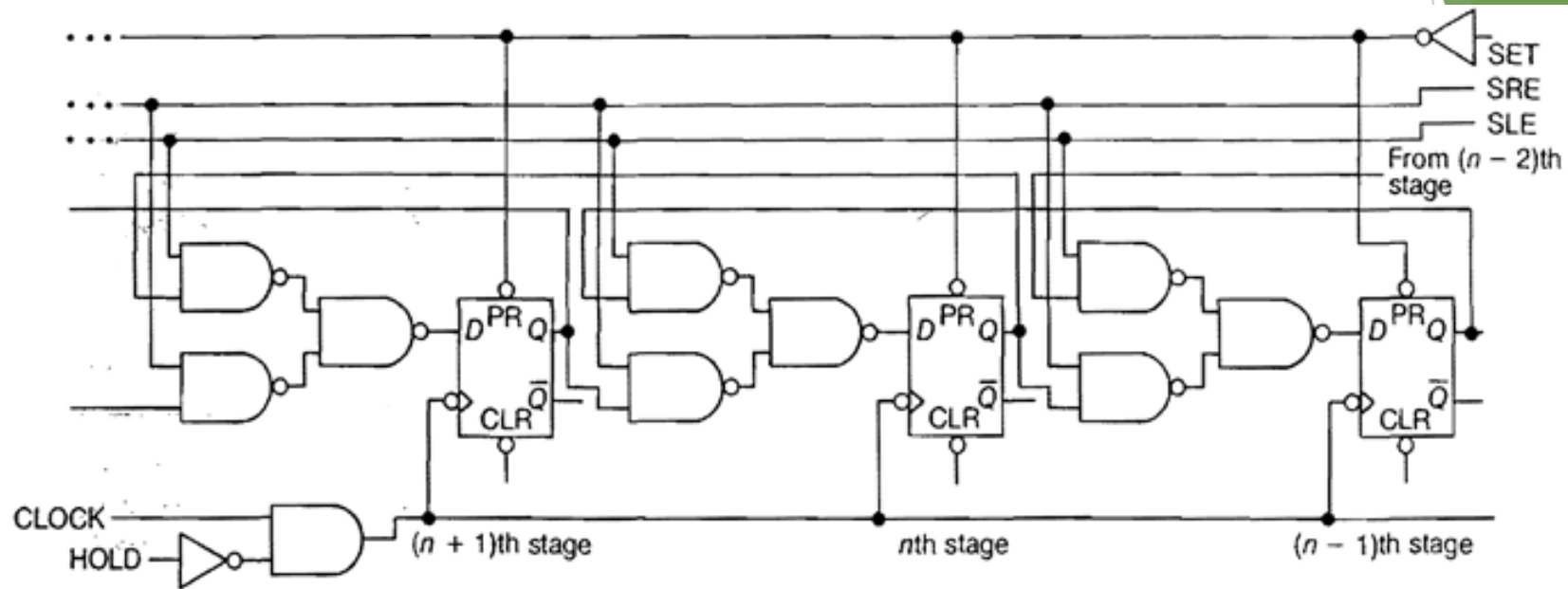
Single register used for both serial-right and serial-left shifts



SRE	SLE	action
0	0	FFs reset
0	1	Shift-left
1	0	Shift-right
1	1	never

Hold	Action
0	Shifts normally
1	Restores old values

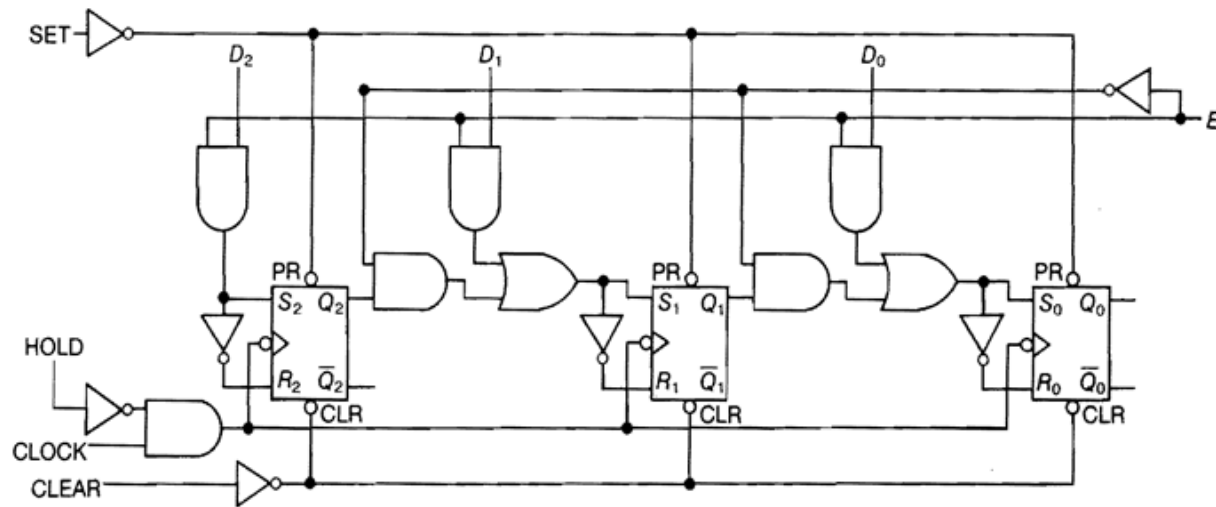
### 3-bit parallel in serial out shift register



E	Action
1	Data loaded
0	Right-shift


Hold	Action
0	Load or shift
1	Restores
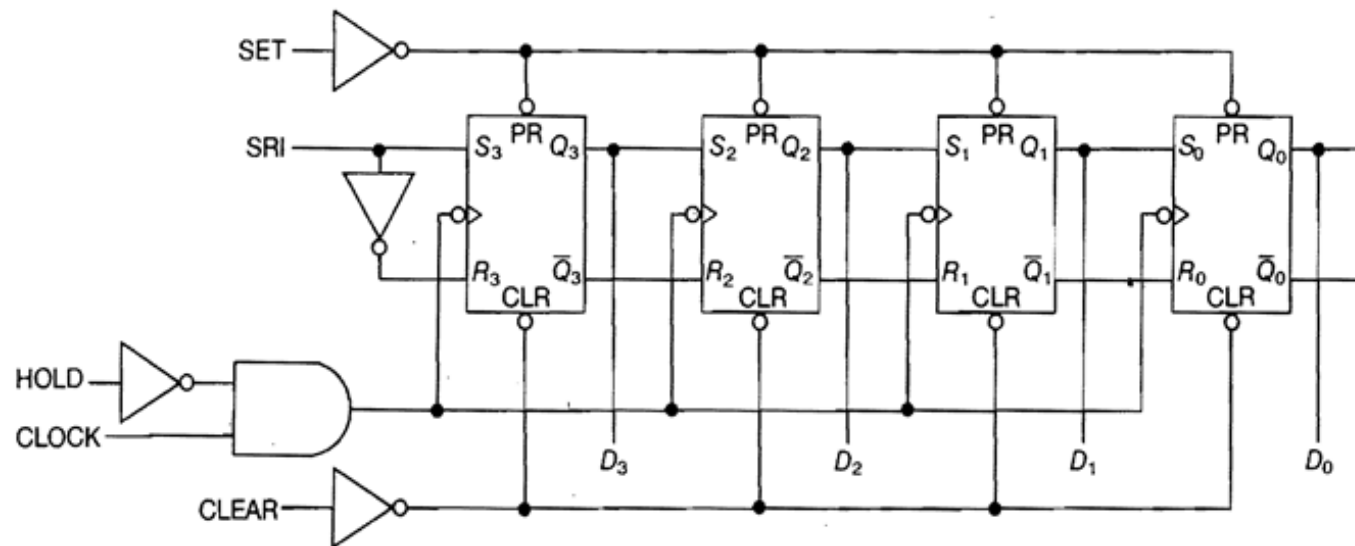
## 4-bit Serial in Parallel out Shift Register





## 4-bit Parallel in Parallel out Shift Register

Load	Action
1	Parallel in/out
0	Serial in/out

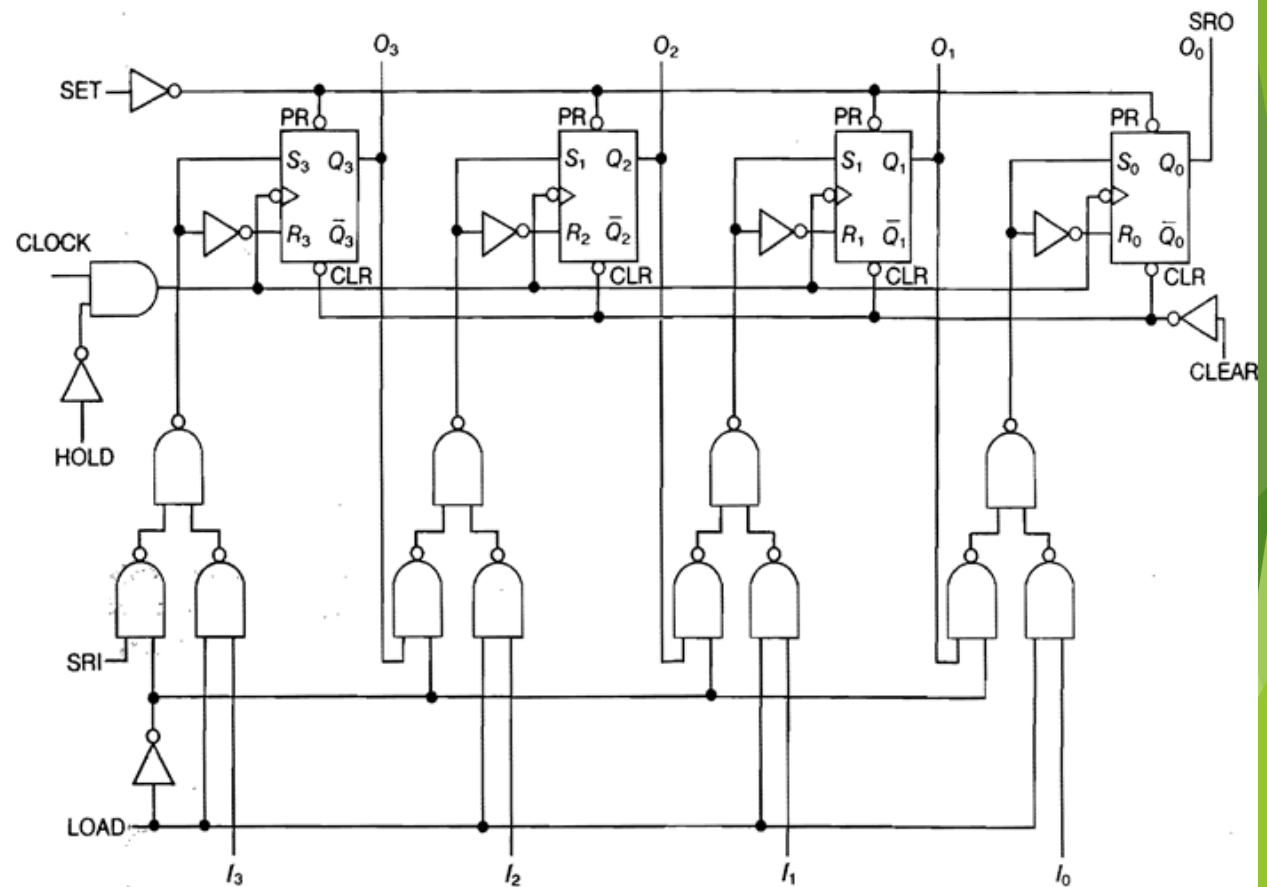

# Universal Shift Register

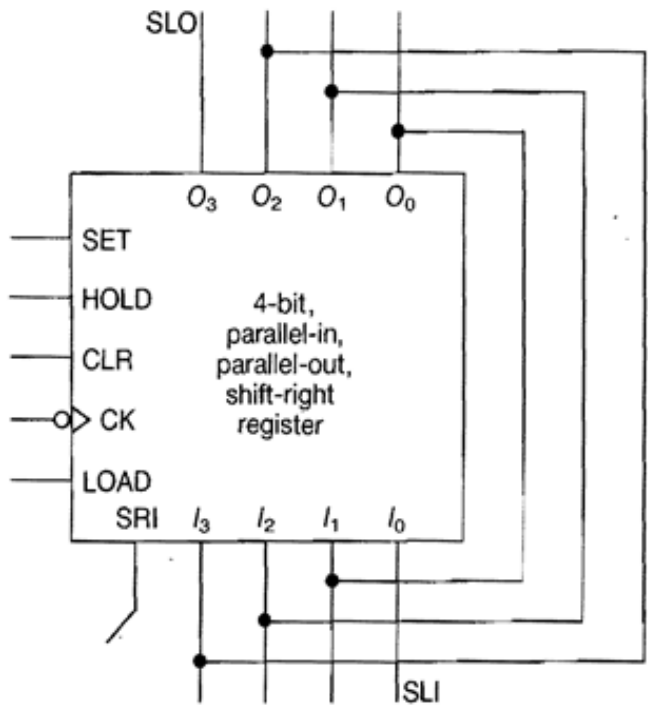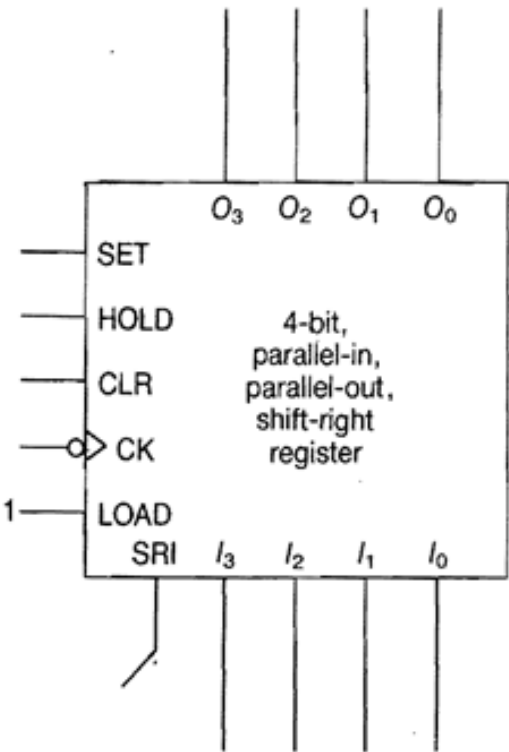

Wired shift-left register

Load	Action
0	Shift-right serial in/out
1	Parallel

# Chapter 5: Design of Asynchronous Sequential Circuits





# Pulse-Mode Circuits:


No clock for state transitions.

Just input pulses, Key boards and Vending machines

No overlapping pulses

Conditions for perfect circuit operation

 
1. Simultaneous input pulses on two or more lines are forbidden. Interval between pulses is large enough for system to return to a stable state.
2. Pulse widths must be sufficient to allow the components to respond to them.



Looks like synchronous without a clock

As long as the previously stated two conditions are met the design of asynchronous circuits will be similar to the synchronous ones

 An example of three nonoverlapping input pulses



### Design Algorithm


1. Get the state diagram. For  $n$ -inputs there be  $n$  transition paths leaving each of the states.
2. Remove redundancies.
3. Assign states and generate state transition table.
4. Get the excitation maps and write down the excitation equations.
5. Draw the circuit diagram.

Example: Design a circuit that receives two inputs  $x_1$  and  $x_2$  and gives an output coincident with the third consecutive  $x_2$  pulse following at least one  $x_1$  pulse.

Forbidden pulses:  $x_1x_2 = 11$

No pulses have occurred

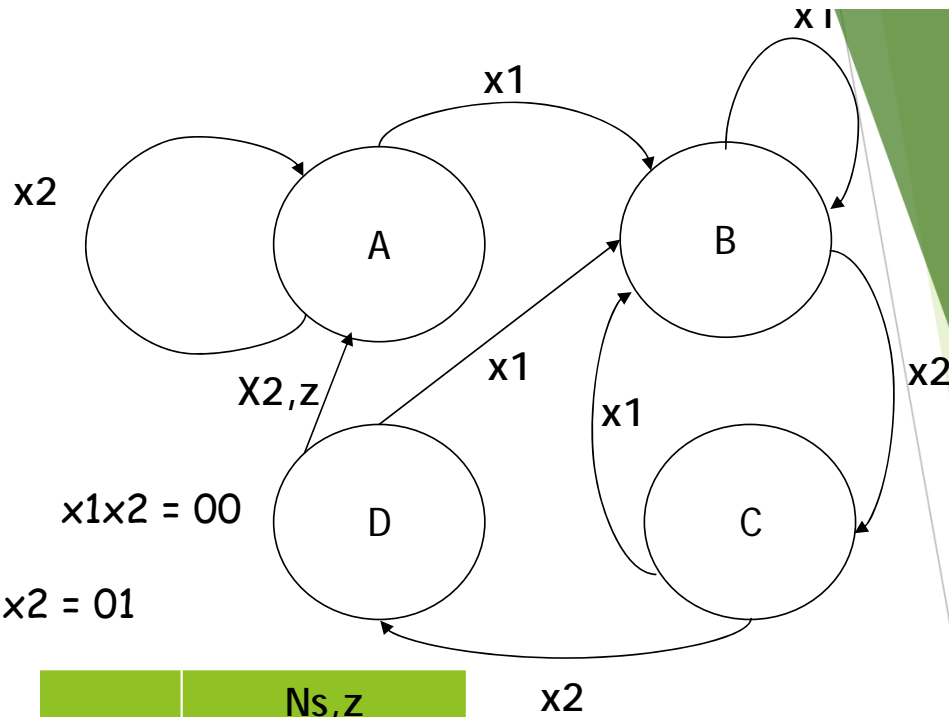Useful pulses  $x_1x_2 = 10$  and  $x_1x_2 = 01$



PS	Ns,z	
	x2	x1
A	A	B
B	C	B
C	D	B
D	A,z	B

PS Q1Q2	Ns,z	
	X2 (01)	X1 (10)
00	00	01
01	11	01
11	10	01
10	00,z	01

Excitation maps:  
T FFs are assumed

PS Q1Q2	Ns,z	
	X2 (01)	X1 (10)
00	00	01
01	11	01
11	10	01
10	00,z	01

Q1Q2	x1	x2
00	0	0
01	0	1
11	1	0
10	1	1

$$T_1 = x_1 Q_1 + x_2 (Q_1 \oplus Q_2)$$

Q1Q2	x1	x2
00	1	0
01	0	0
11	0	1
10	1	0

$$T_2 = x_1 \overline{Q_2} + x_2 Q_1 Q_2$$

Q1Q2	x1	x2
00	0	0
01	0	0
11	0	0
10	0	1


$$z = x_2 Q_1 \overline{Q_2}$$

### Timing diagram of Negative-edge triggered T FFs


$$T1 = x1Q1 + x2(Q1 \oplus Q2)$$

$$T2 = x1\overline{Q2} + x2Q1Q2$$

$$z = x2Q1\overline{Q2}$$

 

 
The HW implementation of the excitation equations




### Example 2:

Design a pulse-mode circuit that satisfies the following requirements. The circuit has two inputs,  $x_1$  and  $x_2$ , and one output,  $z$ . The output pulse is to be produced simultaneously with the last of a sequence of three input pulses if and only if the sequence contained at least two  $x_1$  pulses. After each output a new sequence is looked for.

PS	NS, z	
	$x_1$	$x_2$
A	B	E
B	C	D
C	A,z	A,z
D	A,z	E
E	F	E
F	A,z	D

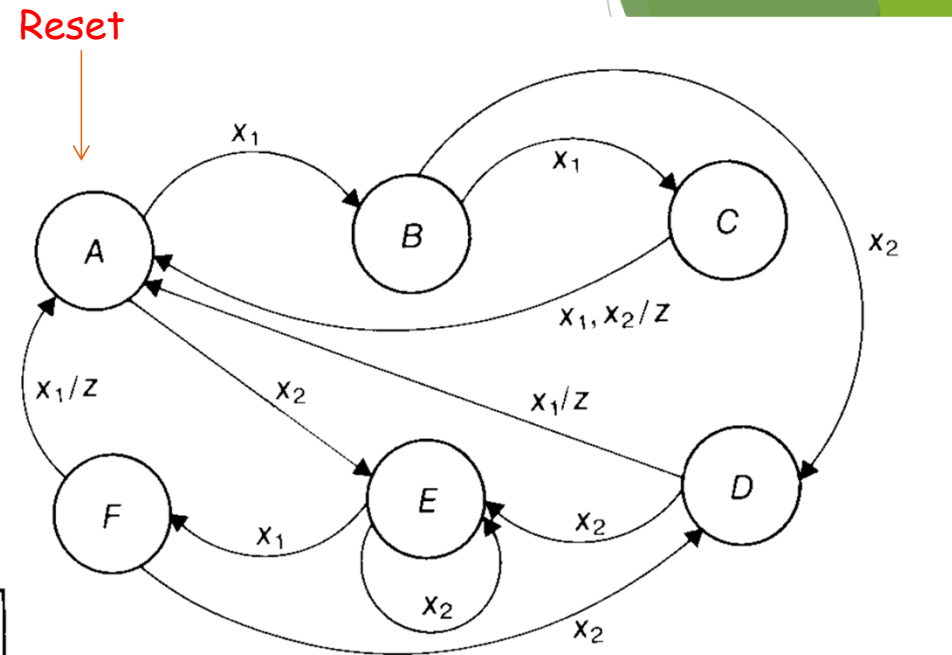

Implication table

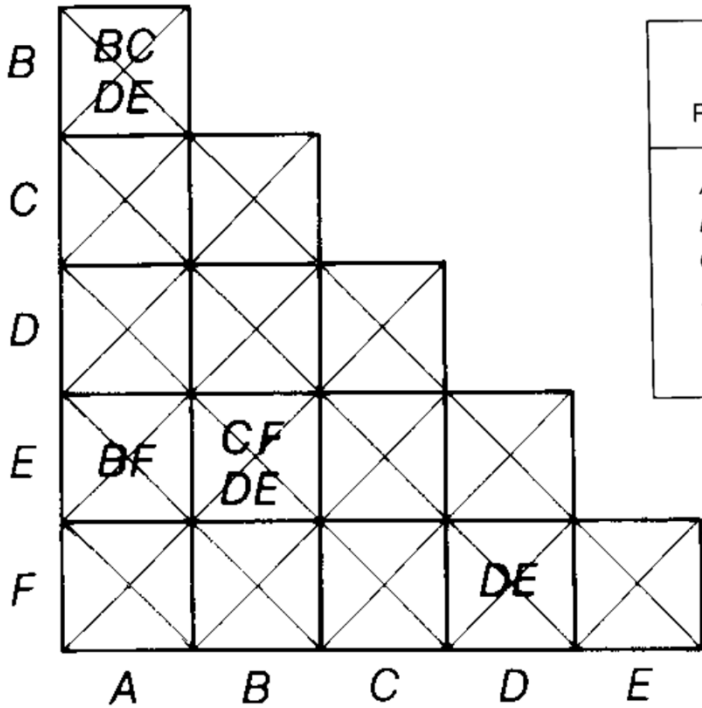

No redundance states

Arbitrary state assignment


PS	NS, z	
	$x_1$	$x_2$
A	B	E
B	C	D
C	A,z	A,z
D	A,z	E
E	F	E
F	A,z	D

- A=000
- B=001
- C=010
- D=100
- E=101
- F=110

State Transition Table

PS	NS, z	
	$Q_1 Q_2 Q_3$	$x_1$
000	001	101
001	010	100
010	000,z	000,z
100	000,z	101
101	110	101
110	000,z	100




 


z

$x_1$

$x_2$

 


$T_1$

 

$T_2$

$x_1$

$x_2$

 

$T_3$

$$z = x_1(Q_2 + Q_1 \bar{Q}_3) + x_2(\bar{Q}_1 Q_2)$$


$$T_1 = x_1(Q_1 \bar{Q}_3) + x_2(\bar{Q}_1 \bar{Q}_2)$$

$$T_2 = x_1(Q_2 + Q_3) + x_2(Q_2)$$

$$T_3 = x_1(Q_3 + \bar{Q}_1 \bar{Q}_2) + x_2(\bar{Q}_1 \bar{Q}_2 + \bar{Q}_2 \bar{Q}_3)$$

PS	NS, z	
$Q_1 Q_2 Q_3$	$x_1$	$x_2$
000	001	101
001	010	100
010	000,z	000,z
100	000,z	101
101	110	101
110	000,z	100

# HW Implementation

 

### Example 3

Analyze the pulse-mode circuit of Figure

The equations of the states and the output are easily written as:


$$S_1 = B + C$$

$$R_1 = D$$

$$S_2 = A\bar{Q}_1$$

$$R = C\bar{Q}_1 + D$$

$$Z = D\bar{Q}_2$$

 

Since it is a pulse-mode circuit the only input conditions that need to be considered are  $ABCD = 1000, 0100, 0010, \text{ and } 0001$ .



$$S_1 = B + C$$

$$R_1 = D$$

$$S_2 = A\bar{Q}_1$$

$$R_2 = C\bar{Q}_1 + D$$

$$Z = D\bar{Q}_2$$

  

PS		NS. z			
Q <sub>1</sub> Q <sub>2</sub>		A	B	C	D
P	00	01,0	10,0	10,0	00,1
Q	01	01,0	11,0	10,0	00,0
R	11	11,0	11,0	11,0	00,0
S	10	10,0	10,0	10,0	00,1