



# COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electronics and Communications

Lecturer : Prof. Dr. Mohamed El-Banna

TA: Amr El-Helw


Course : Electronic Circuits II

Course Code: EC 432

Sheet 4

1. The data sheet of the SN7400 quad 2-input NAND gate of TTL family provide the following:
  - Logic-1 input voltage required at both terminals to ensure a logic-0 level at the output : MIN (minimum) 2 V.
  - Logic-0 output voltage required at either input terminal to ensure a logic-1 level at the output: MAX (maximum) 0.8 V.
  - Logic-1 output voltage: MIN 2.4 V, TYP (typical) 3.3 V.
  - Logic-0 output voltage: TYP 0.22 V, MAX 0.4 V.
  - Logic-0-level supply current: TYP 12 mA, MAX 22 mA (for the entire package)
  - Logic-1-level supply current: TYP 4 mA, MAX 8 mA (for the entire package)
  - Propagation delay time to logic-0 level: TYP 7 ns, MAX 15 ns.
  - Propagation delay time to logic-1 level: TYP 11 ns, MAX 22 ns.
  - a- Find the noise margin in both the 0 and 1 states.
  - b- Assuming that the gate is in the 1 state 50% of the time and in the 0 state 50% of the time, find the average static power dissipated in a typical gate. The power supply voltage is +5 V.
  - c- Assuming that the gate drives a capacitance  $C_L=45$  pF and is switched at 1-MHz rate, find the dynamic power dissipation per gate using the typical values of the logic 1 and 0 levels at the output.
  - d- Find the typical value of the gate delay-power product (neglecting the dynamic power dissipation)
2. A logic inverter having a negligible static power dissipation is switched at a rate of 1 MHz. If the inverter is operated from a 10-V power supply and drives a 50-pF load capacitance, find the dynamic power dissipation and the average current drawn from the power supply. Assume that the output levels are close yo 0 and 10 V.
3. An enhancement-load inverter having  $(W/L)_1=3$  and  $(W/L)_2=1/3$  is fabricated with a technology for which the minimum practical transistor dimension (length or width) is  $5 \mu\text{m}$ . Find the area occupied by this inverter and the value of its  $K_R$ . If  $K_R$  is to be quadrupled, find the ratio  $(W/L)$  for each device so that silicon area required by the inverter is the minimum possible.
4. Consider an enhancement-load inverter having  $V_{t0}=1$  V,  $(W/L)_1=3$ ,  $(W/L)_2=1/3$ ,  $\mu_n c_{ox}=20 \mu\text{ A/V}^2$ ,  $2\phi_f = 0.6$  V,  $\gamma = 0.5\text{V}^{1/2}$  and  $V_{DD}=5$  V.
  - a- Neglecting the body effect, find the critical points of the voltage transfer characteristic, and hence the noise margin.
  - b- Taking the body effect into account, find the modified values of  $V_{OH}$  and  $NM_H$ .
  - c- Find the inverter current in both states, and hence find the average static power dissipation.

 5. Consider the DTL gate circuit shown in the figure below and assume that  $\beta(Q_2) = \beta(Q_3) = 50$ .
- When  $v_i = 0.2\text{ V}$ , find the input current.
  - When  $v_i = +5\text{ V}$ , find the base current of  $Q_3$ .



6. The figure below shows the circuit that guarantees the reference voltage  $V_R$ . Assuming that the voltage drop across each of  $D_1$  and  $D_2$ , and the base-emitter junction of  $Q_1$  is  $0.75\text{ V}$ , calculate the value of  $V_R$ . Neglect the base current of  $Q_1$ .

